

## SIMULATION OF UNCONTROLLED RECTIFIER ON MATLAB / SIMULINK

**Objective:** The objective of this experiment is to study the operation of single-phase uncontrolled rectifiers using MATLAB/SIMULINK.

### Parameter:

Parameter	Value
Input voltage	230 V, 50 Hz
Source Inductance	10 mH
Case 1: Load	20 $\Omega$
Case 2: Load	20 $\Omega$ in series with 20 mH Inductance
Case 3: Load	20 $\Omega$ in series with 200 mH Inductance
Case 4: Load with Source Inductance	20 $\Omega$ in series with 200 mH inductance & $L_s = 10\text{mH}$

**Theory:** Rectifier is a AC to DC converter. In this converter we are using diode so we do not have controlled output so it is an uncontrolled rectifier.

Avg. Output Voltage:

$$V_o = \frac{2V_m}{\pi}$$

Where  $V_m$  is maximum input voltage.

Overlap angle  $\mu$  (when source inductance present):

$$\cos(\alpha + \mu) = \cos\alpha - \frac{2\omega L_s I_o}{V_m}$$

### Design procedure and final design parameters obtained:

- In positive half cycle of input voltage  $D_1$  and  $D_2$  conducts, so

$$V_o = V_{in}$$

- In negative half cycle of input voltage  $D_3$  and  $D_4$  conducts, so

$$V_o = -V_{in}$$

- Here we are taking 100 Samples for each Time period So, Sampling frequency is 100 times of maximum frequency(100Hz).

So, Sampling Time Period = 100 $\mu$ Sec.

## Circuit Diagram and Theoretical Waveforms:

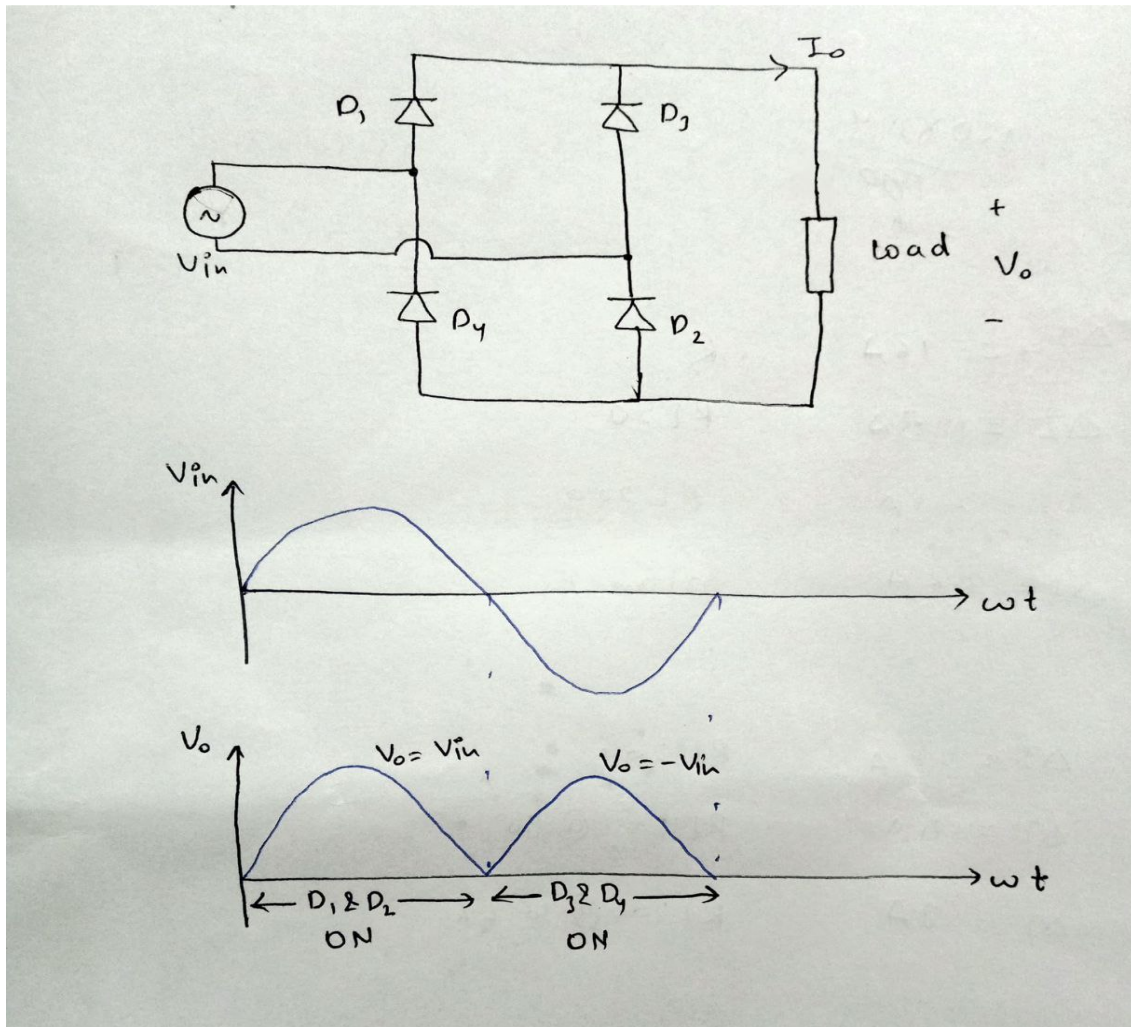


Fig.1 Theoretical Diagram of Uncontrolled Rectifier

## Simulation Model:

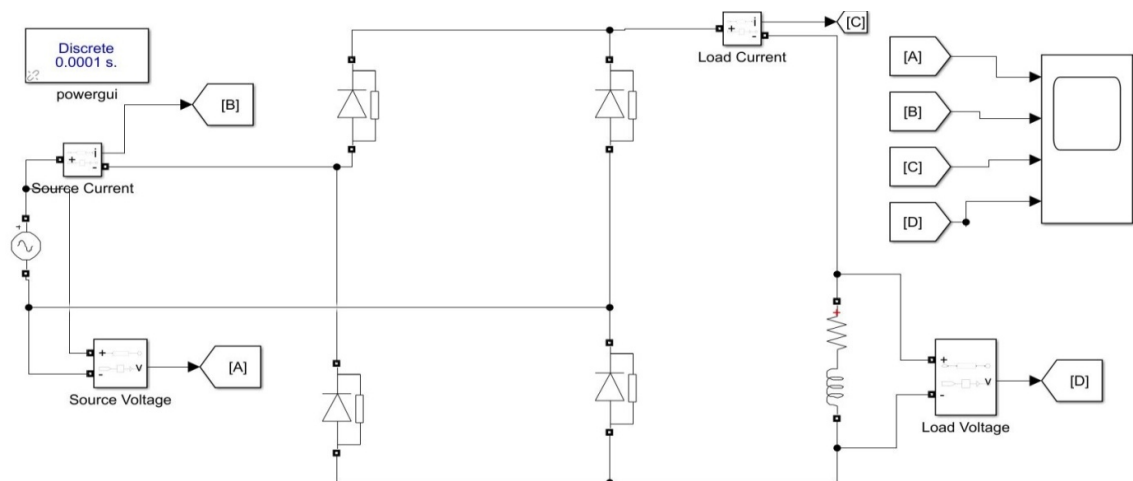


Fig.2 Simulation model without source inductance


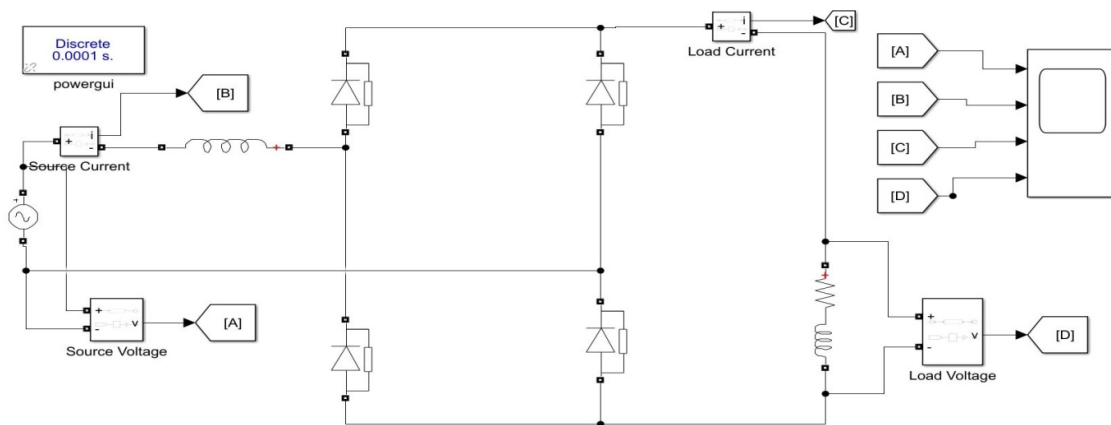


Fig.3 Simulation model with source inductance

## Waveforms and Results:


### Case 1 : Load 1 ( $R=20\Omega$ )

	Theoretical	Practical
Avg. Output Voltage	207V	206V
Ripple in Output Current	16.25A	16A

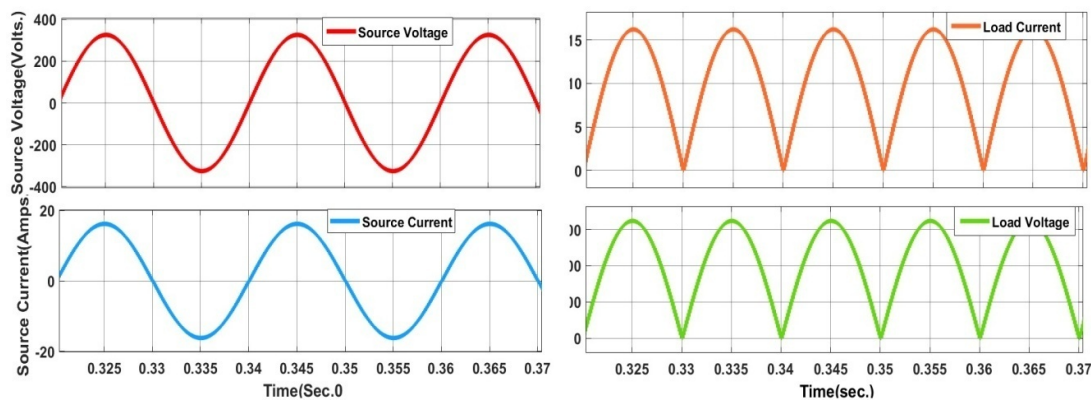


### Case 2 : Load 2 ( $R=20\Omega$ & $L=20\text{mH}$ )

	Theoretical	Practical
Avg. Output Voltage	207V	206V
Ripple in Output Current	12.3A	12.3A

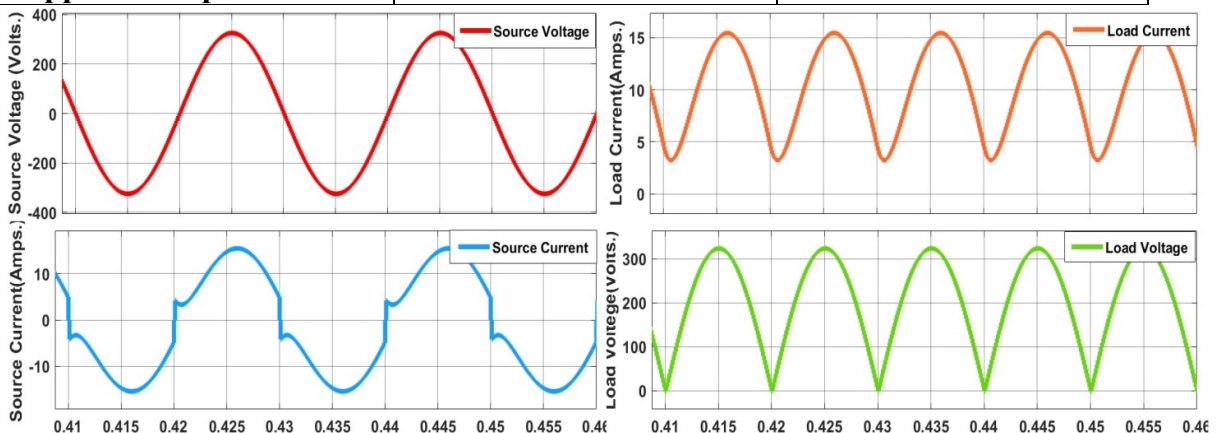


**Case 3 : Load 3 ( $R=20\Omega$  &  $L=200\text{mH}$ )**

	Theoretical	Practical
<b>Avg. Output Voltage</b>	207V	206V
<b>Ripple in Output Current</b>	3.1A	3.8A

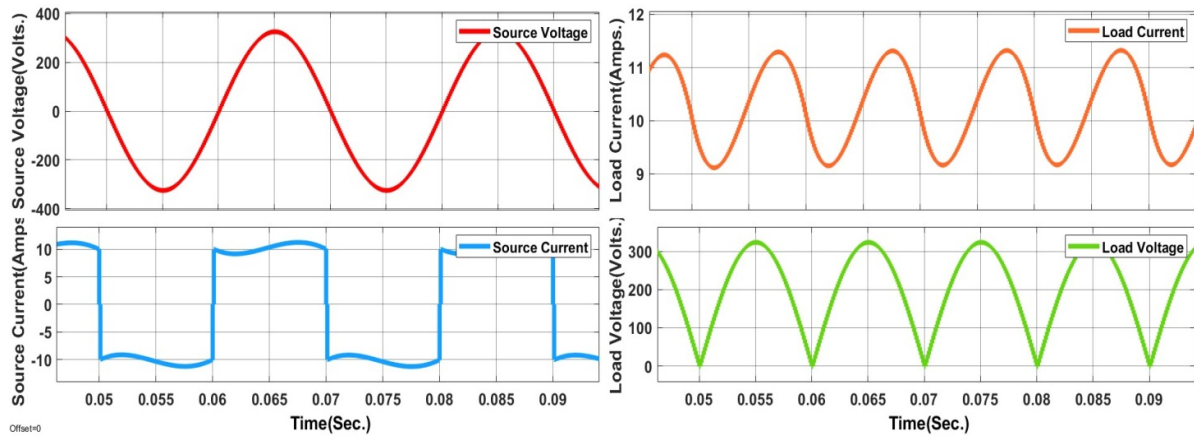

**Case 4 : Load 3 ( $R=20\Omega$  &  $L=20\text{mH}$ ) with Source Inductance ( $L_m$ )**

	Theoretical	Practical
<b>Avg. Output Voltage</b>	187V	185.4V
<b>Ripple in Output Current</b>	2.6A	3A
<b>Overlap Angle</b>	$36.95^\circ$	$32.5^\circ$

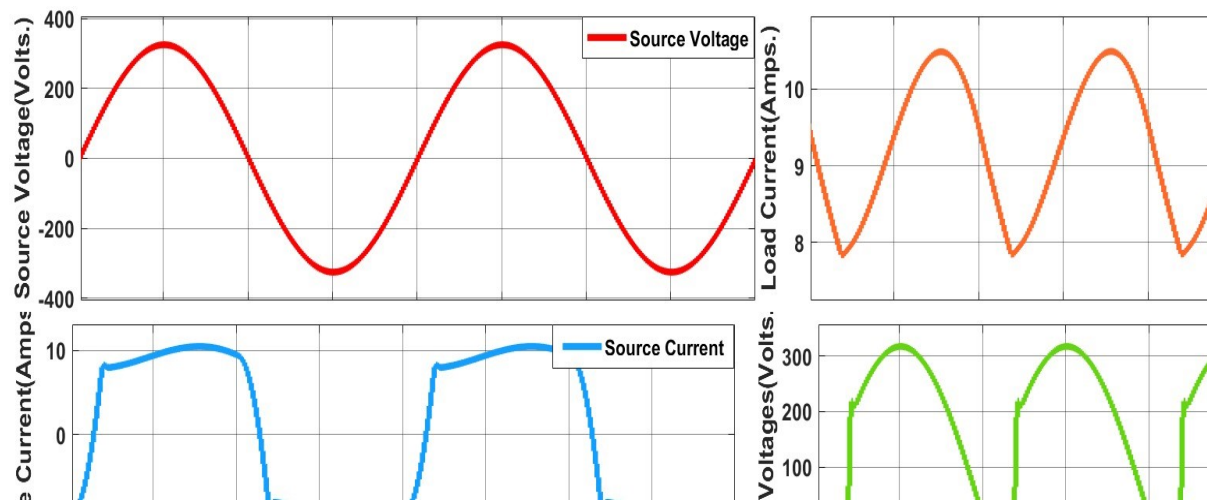

**Result:** Due to the source inductance there is reduction in output voltage observed.

## SIMULATION OF PHASE CONTROLLED RECTIFIER ON MATLAB / SIMULINK

**Objective:** The objective of this experiment is to study the operation of single-phase controlled rectifiers using MATLAB/SIMULINK.

**Parameters:**

Parameter	Value
Input voltage	230 V, 50 Hz
Source Inductance	10 mH
Case 1: Load & Firing angle $\alpha = 30$	20 $\Omega$ in series with 200 mH Inductance
Case 2: Load & Firing angle $\alpha = 60$	20 $\Omega$ in series with 200 mH Inductance
Case 3: Load, $L_s$ & $\alpha = 30$	20 $\Omega$ in series with 200 mH inductance & $L_s = 10\text{mH}$

**Theory:** Rectifier is a AC to DC converter. In this converter we are using diode so we do not have controlled output so it is an uncontrolled rectifier.

Avg. Output Voltage:

$$V_o = \frac{V_m}{\pi} (1 + \cos \alpha) \quad \text{valid for R load}$$

Where  $V_m$  is maximum input voltage.

Avg. Output Voltage:

$$V_o = \frac{2V_m}{\pi} \cos \alpha \quad \text{valid for continuous conduction}$$

Overlap angle  $\mu$  (when source inductance present):

$$\cos(\alpha + \mu) = \cos \alpha - \frac{2\omega L_s I_o}{V_m}$$

**Design procedure and final design parameters obtained:**

- In positive half cycle of input voltage, Thyristor  $T_1$  and  $T_2$  conducts, so

$$V_o = V_{in}$$

- In negative half cycle of input voltage, Thyristor  $T_3$  and  $T_4$  conducts, so


$$V_o = -V_{in}$$

- Here we are taking 100 Samples for each Time period So, Sampling frequency is 100 times of maximum frequency(100Hz).


So, Sampling Time Period = 100 $\mu$ Sec.



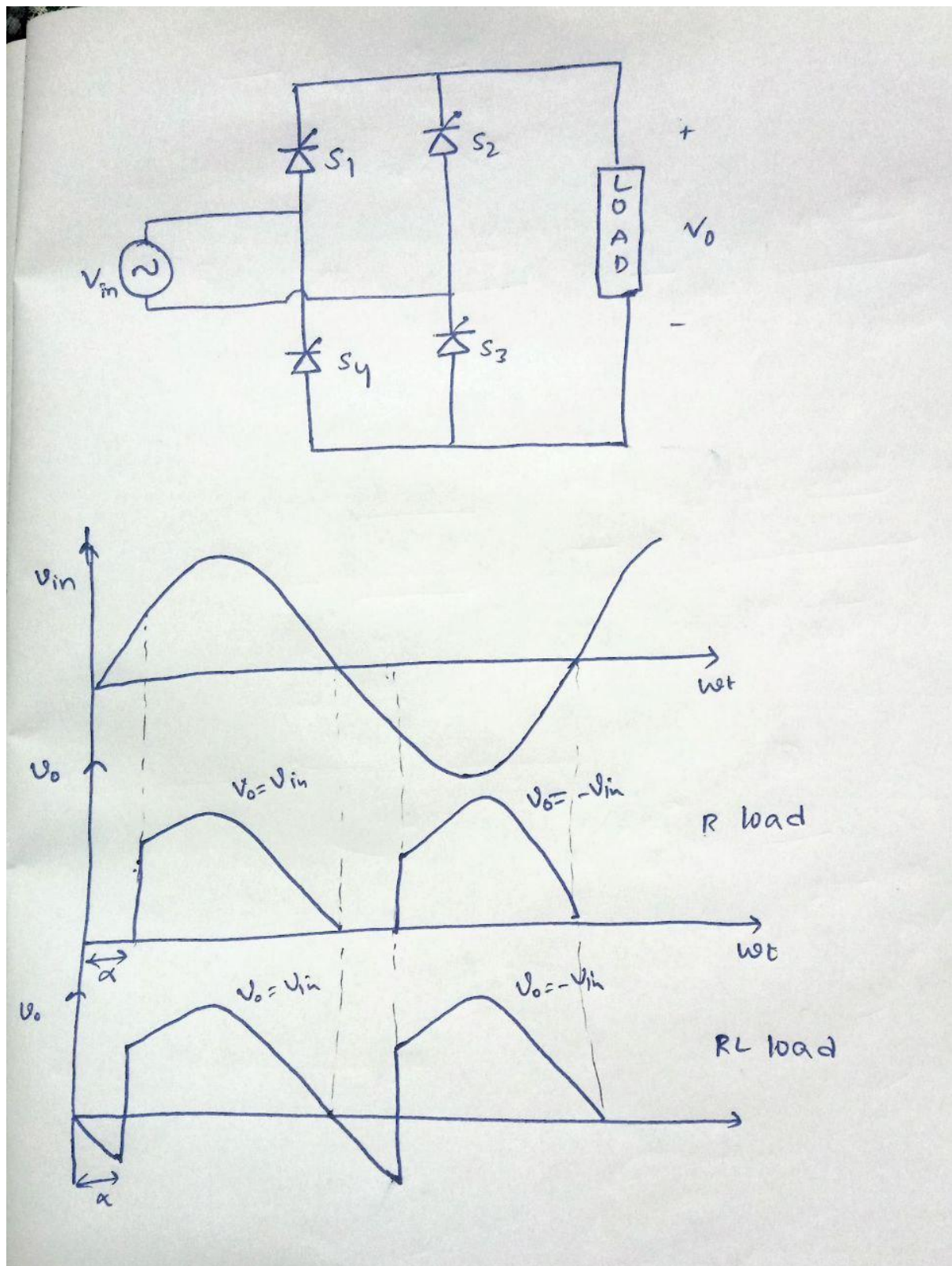
### Circuit Diagram and Theoretical Waveforms:




## Simulation Model:

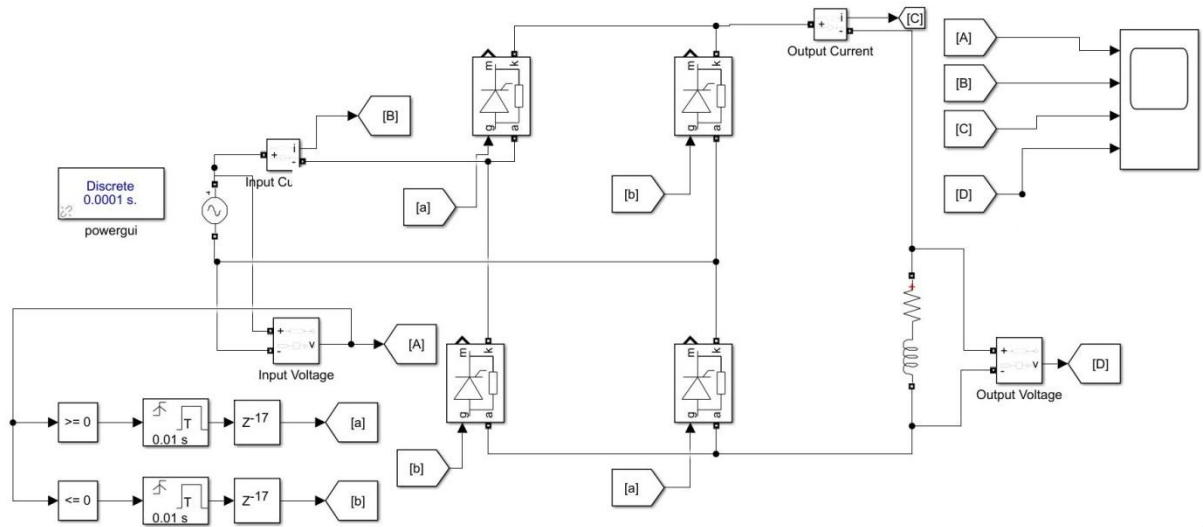

**Fig.2 Simulation model without source inductance ( $\alpha=30^\circ$ )**

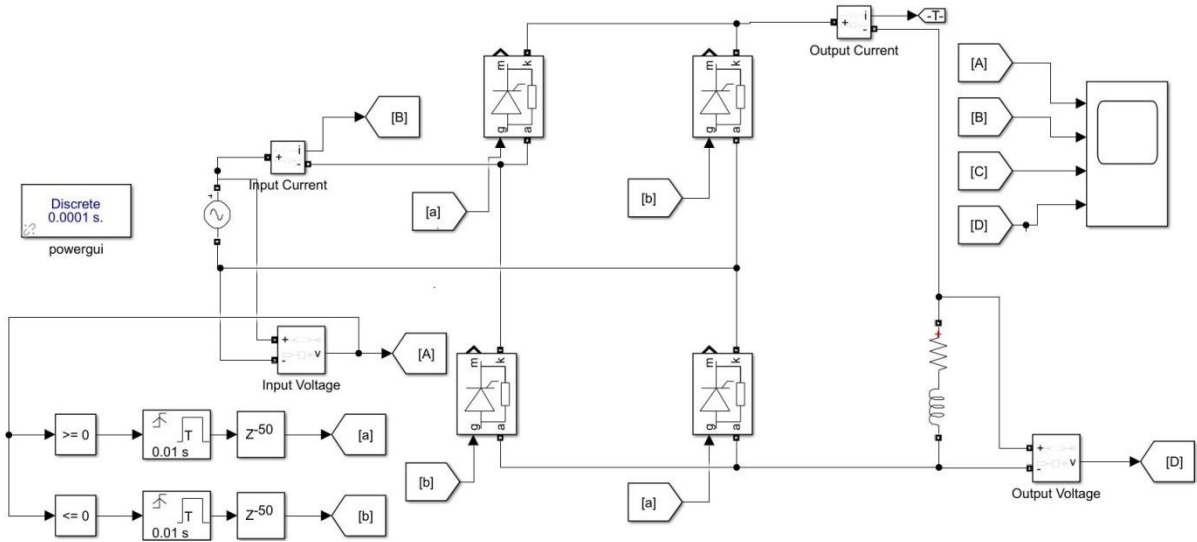

**Fig.3 Simulation model without source inductance ( $\alpha=90^\circ$ )**

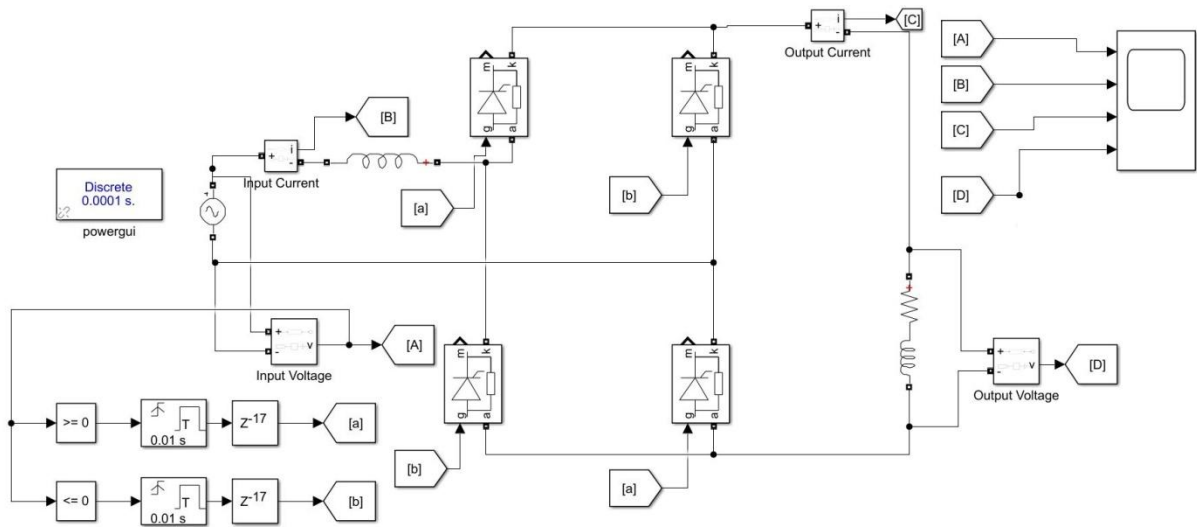


**Fig.3 Simulation model with source inductance ( $\alpha=30^\circ$ )**
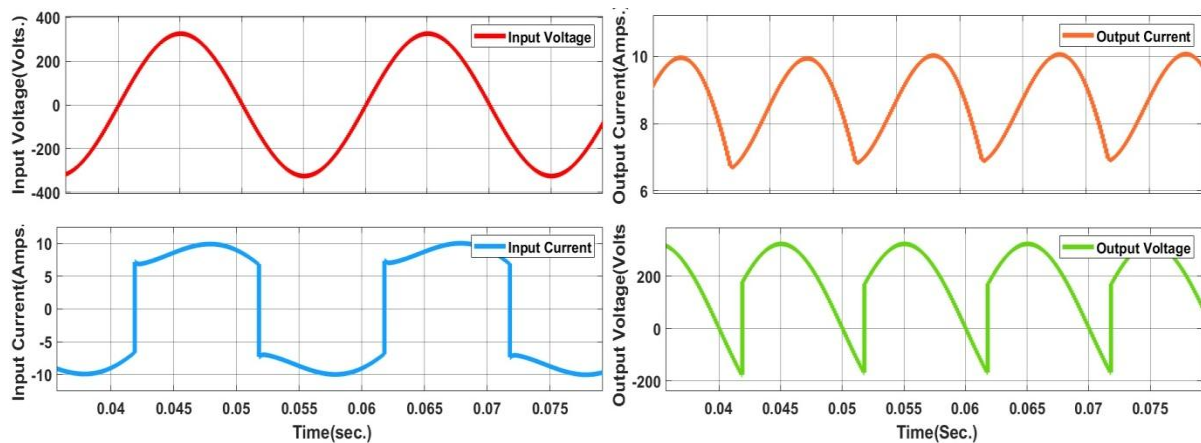
## Waveforms and Results:


**Case 1:** Load 1 ( $R=20\Omega$  &  $L=200\text{mH}$ ) ( $\alpha=30^\circ$ )

	Theoretical	Practical
<b>Avg. Output Voltage</b>	179.33V	177.5V
<b>Ripple in Output Current</b>	8.96A	10.2A



**Case 2 :** Load 2 ( $R=20\Omega$  &  $L=200\text{mH}$ ) ( $\alpha=90^\circ$ )


	Theoretical	Practical
<b>Avg. Output Voltage</b>	103.53V	101.2V
<b>Ripple in Output Current</b>	5.17A	7.3A

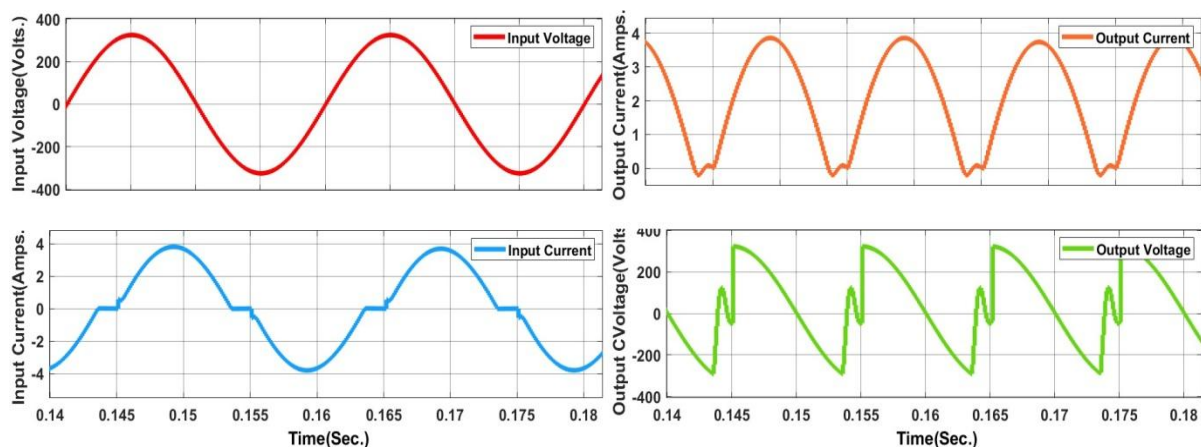



**Case 4 :** Load 3 ( $R=20\Omega$  &  $L=200\text{mH}$ ) with Source Inductance ( $L_s$ ) ( $\alpha=30^\circ$ )

	Theoretical	Practical
<b>Avg. Output Voltage</b>	166V	164.8V
<b>Ripple in Output Current</b>	3.25A	3A
<b>Overlap Angle</b>	$9^\circ$	$12^\circ$

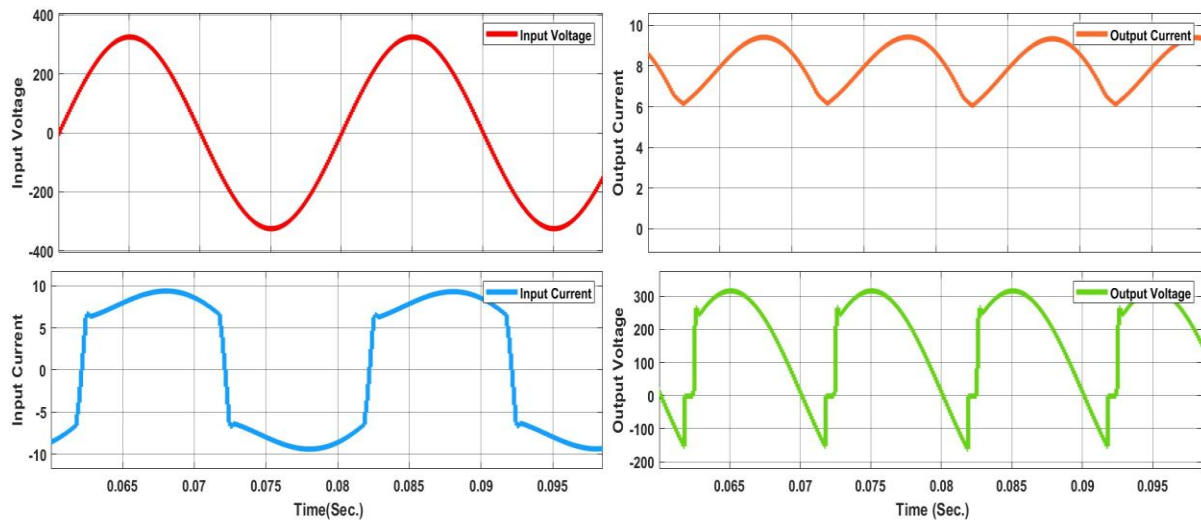

**Result:** Due to the source inductance there is reduction in output voltage observed.